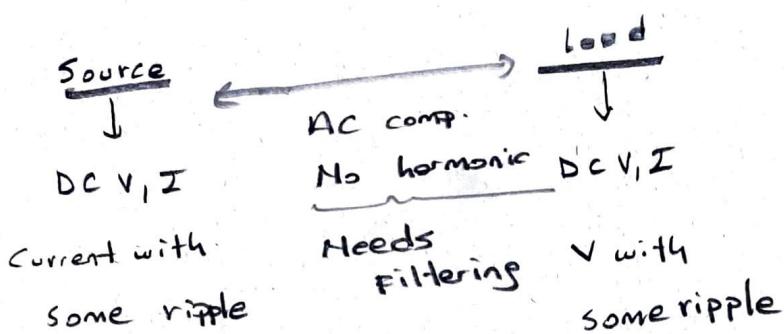


$$D = t_{on} \cdot f_s = \frac{t_{on}}{T}$$



widely used low V, P

Synchronous version and resonant derivatives provide EFF.

CCM → Inductor current + always

DCM → " " remains 0 for some time.

$$V_o = D \cdot V_s$$

!! Sizing components

Mosfet → V_{DS} and I_d

Diode → V_{FMM} , I_f

inductor → L and I_{pk}

Coups → C, V and I_{VMS}

use critical inductance



$$(I_{Lmin} = V_o \cdot \left(\frac{1}{R} - \frac{(1-D)}{2L_f} \right))$$

$$I_{Lmax} = V_o \left(\frac{1}{R} + \frac{(1-D)}{2L_f} \right)$$

$$L_C = \frac{(1-D_{max})}{2 + \frac{1}{R}}$$

$$\boxed{\text{For best } I_{Lmin} = 0}$$

$$L > 1.05 \times b_2$$

$f \uparrow \Rightarrow$ small L

$$D \Rightarrow V_{\text{switch-max}} = V_{\text{in max}} + \underbrace{V_f}_{\text{max forward}}$$

Safety factor 1.20

Mosfet $\Rightarrow V_{DS\text{ max}}$

current rating (Mosfet) = Average value

$$I_L = I_S + I_D$$

$$\rightarrow I_{\text{switch-max}} > I_{\text{omax}} \times D_{\text{max}}$$

Mosfet rating ex

14A, 500V, $R_{DS(\text{on})}$ \Rightarrow N channel power mosfet

Diode rating

$V_{ZRM} \Rightarrow$ Peak inverse voltage

$$V_{ZRM} = V_{\text{in max}} + \underbrace{V_{GW}}_{\text{calc at load current}} \Rightarrow 1.20 \text{ ! safety factor}$$

Diode current Rating \Rightarrow schottky rectifier diode

$$\bar{I}_+ > \overline{I_{\text{omax}}} (1 - D_{\text{min}})$$

Sizing Cap

V rating

$$\text{ideally } V_{C\text{max}} = V_o + \Delta V_o / 2$$

Real C has ESR Eq. series R

$$\text{output } V \text{ ripple} = ESR \times \Delta I_o$$

Reduce ESR \Rightarrow Parallel caps

$$\text{or } \Delta I_o \Rightarrow \uparrow f_{\text{req}}, \uparrow L$$

Min C (output)

$$C = \frac{1 - D_{\min}}{8 L_f^2 (\Delta V_o/V_o)} \rightarrow \text{Percent } V_{o\text{pp}}$$

RMS current

$$i_{\text{crms}} = \frac{(1 - D_{\min}) V_o}{2\sqrt{3} L_f}$$

Min C (input)

$$C = \frac{(1 - D) \cdot D \cdot I_{\max}}{+ \cdot \Delta V_{\text{in}}}$$

V rating (input)

$V_{c\max} = V_{\text{in}\max} \rightarrow \text{ideal}$
with ESR \rightarrow caps loss

I_c RMS (input)

$$\sqrt{\left[I_o \sqrt{D} \sqrt{1 + \frac{\Delta I_o}{2I_o}} \right]^2 - (D I_o)^2}$$

Summarize


$$I_{s\max} > I_{\max} \cdot D_{\max}$$

$$V_{s\max} = V_{\text{in}\max}$$

$$I_{L\max} = V_o \left[\frac{1}{R_{\min}} + \frac{1 - D_{\min}}{2L_f} \right]$$

$$I_C = \frac{(1 - D_{\max}) \cdot D_{\max}}{2f}$$

V_s

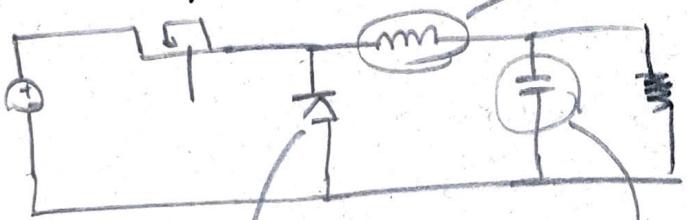

$$I_f > I_{\max} \cdot (1 - D_{\min})$$

$$V_{r\text{m}} = V_{\text{in}\max}$$

$$C = \frac{1 - D_{\min}}{8 L_f^2 (\Delta V_o/V_o)}$$

$$V_{c\max} = V_o + \Delta V_o/2$$

$$i_{\text{crms}} = \frac{(1 - D_{\min}) V_o}{2\sqrt{3} L_f}$$

Losses

static loss of Mosfet

switching loss of Mosfet

MOSFET Gate drive loss

static loss of diode

switching loss of diode

L copper loss

C ESR loss

Static loss for MOSFET RDS on

$$P_{\text{static}} = \left[I_o \sqrt{D} \sqrt{\left(1 + \frac{\Delta i_L}{2I_o}\right)^2} \right] R_{DSS}$$

$$P_{\text{switching}} = \frac{2D V_{in}}{6T} (t_{on} + t_{off})$$

$$\left. \begin{aligned} P_{Coss} &= \frac{1}{2} C_{oss} V_{in}^2 T \\ P_{gate} &= \frac{1}{2} Q_{gate} V_{gate} T \end{aligned} \right\} \begin{array}{l} \text{switching loss of load} \\ \text{gate drive loss} \end{array}$$

Static loss diode (forward)

$$P_{\text{forward}} = V_f \times I_f + I_f^2 \cdot R_d$$

$$(1-D) I_o$$

$$\sqrt{\frac{1-D}{3} [I_{max}^2 + I_{min}^2 + I_{max} I_{min}]}$$

$$P_{\text{reverse}} = V_r I_r (1-D)$$

Switching loss of diode

$$\text{Turn on} \Rightarrow P_{on} = 0.4 (V_{fP} - V_f) + \frac{1}{2} I_f \cdot t_{on}$$

peak forward forward
recovery time

Copper Loss

$$P_L = I_c^2 \cdot R_L \rightarrow I \times \sqrt{1 + \frac{1}{3} \left(\frac{\Delta i_L}{2I}\right)^2}$$

$$\text{Core loss/unit} = k_1 \times B^{k_2} + k_3$$

COPS Loss

$$\tilde{I}_c^2 + \tilde{I}_{SR}^2 \rightarrow \frac{\Delta i_L}{2\sqrt{3}}$$